



Design notes:

1N4007 diode is used to prevent interference from unwanted voltage feedback into relay which causes unwanted energizing of relay coil and subsequent relay clicking when not required.

Audible Lights on reminder (Version 2) By Theunis Visser

Date: 14-04-2010

Checked date: 14-04-2010

Rework date: 19-04-2010